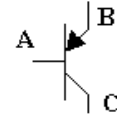


Quiz 1 Review

1

1



Name: _____


A: _____

B: _____

C: _____


2

2

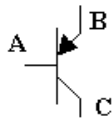Name: PNP TransistorA: BaseB: EmitterC: Collector

3

3

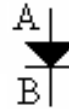

Name: _____

A: _____

B: _____

4

4

Name: DiodeA: AnodeB: Cathode

5

5

How is a Thyristor different than a Transistor?

How is it started?

Does it limit the current flow when on?

When does it turn off?

6

6

How is a Thyristor different than a Transistor?

A Thyristor has 2 operation states Blocking and Conduction.

How is it started?

Applying Proper Gate Voltage with a proper voltage Drop

Does it limit the current flow when on?


No

When does it turn off?

When the current drops below the Holding Current

7

7

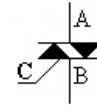

Name: _____


A: _____

B: _____

C: _____

8

8

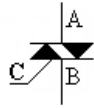

Name: TRIAC


A: MT2

B: MT1

C: Gate

9

9

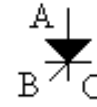

Name: _____

A: _____

B: _____

C: _____

10

10



Name: SCR

A: Anode


B: Gate

C: Cathode

11

11

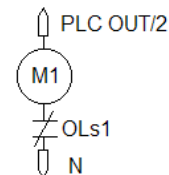
Sketch the protective device that would reduce the inductive kick produced by the coil when it is turned off.



12

12

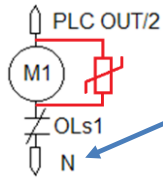
Sketch the protective device that would reduce the inductive kick produced by the coil when it is turned off.



Hint: The Coil goes to Neutral, this is an AC Output so and MOV is used.

13

13

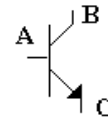

Name: _____


A: _____

B: _____

C: _____

14

14

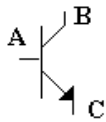

Name: **NPN Transistor**

A: **Base**


B: **Collector**

C: **Emitter**

15

15


Name: _____

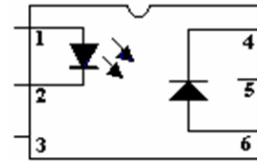

16

16


Name: **Opto-Diode**

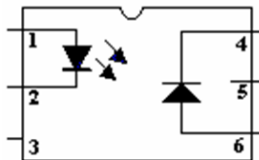

17

17


Name: _____

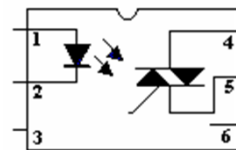

18

18


Name: **Opto-TRIAC**

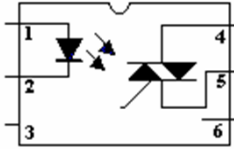

19

19


Name: _____

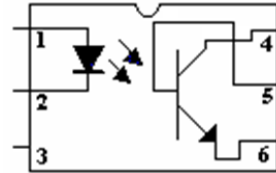

20

20


Name: **Opto-Transistor**

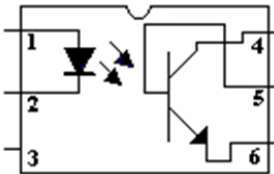

21

21


Name: _____

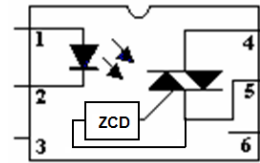

22

22

Name: **Opto-TRIAC w/ ZCD**

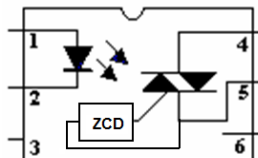


23

23

Sketch the protective device that would reduce the inductive kick produced by the coil when it is turned off.

DC Sinking

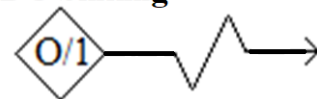


24

24

Sketch the protective device that would reduce the inductive kick produced by the coil when it is turned


off.

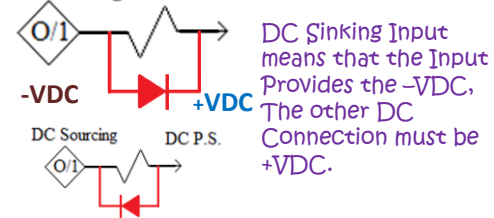

25

25

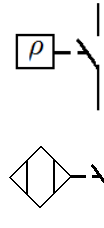
What are these symbols, what are the contact conditions and show the NEMA symbols



26

26

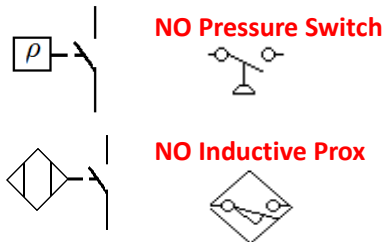
What are these symbols, what are the contact conditions and show the NEMA symbols



27

27

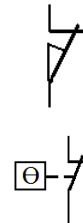
What are these symbols, what are the contact conditions and show the NEMA symbols



28

28

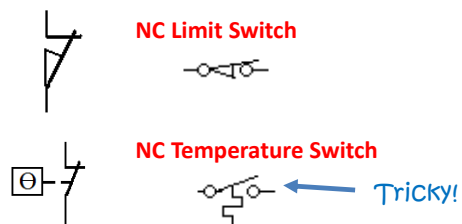
What are these symbols, what are the contact conditions and show the NEMA symbols



29

29

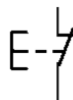
What is this symbol, what are the contact conditions and show the NEMA symbol



30

30

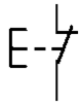What is this symbol, what are the
contact conditions and show the
NEMA symbol



Normally Closed Pushbutton



31