EET 272 Quiz 2 Review

Chapters 23-27 Across The Line, XL, R, Autotransformer and Y-∆ Starting

1

3

What is the difference between Open and Closed Transitioning? (Think of the applied voltage) In Closed Transitioning the motor is never disconnected from power when starting, in Open Transitioning the Motor will coast for a short time between stages. If Resistor or Inductor (R/XL) Starting is used to start a motor, how are they removed at the right time? Specifically, what do the contacts do?

What is the difference between Open and Closed Transitioning? (Think of the applied voltage)

If Resistor or Inductor (R/XL) Starting is used to start a motor, how are they removed at the right time? Specifically, what do the contacts do? They are placed <u>in series</u> with the motor and <u>shorted</u> to apply full power





6

2

What is "Across the Line" Starting? Applying full power at start (AKA DOL or Direct-On-Line)

On what kinds of motors is it used? Small AC and DC why is arcing in AC not as bad as DC?

8

Why is arcing in AC not as bad as DC?

AC Voltage and Current has Zero Crossings What advantage does XL starting offer, other than reduced heat (Inductive Principle)? ...

10

What advantage does XL starting offer, other than reduced heat (Inductive Principle)? Inductors oppose changes in current and inrush is a large change in current. Why might Across the Line Starting not be a good option? Think of the Power-System.

12

7



What is the main advantage of a **series-connected** motor?

High torque at low speeds (Excellent Starting Torque)

What is the main advantage of a shunt-connected motor?

What is the main advantage of a shunt-connected motor?

Excellent Speed Control The same speed no-load to full load

19

What is the danger of a seriesconnected motor?

20

What is the danger of a seriesconnected motor?

No Speed Control

Will over-speed to death with no load

21



22

How does Autotransformer Starting differ from R/XL Starting? (What is reduced?)

















How is the direction of a 3-Phase Motor reversed? Swap any 2 of the 3 "T" Leads 31 32 32

When a motor is first started, or has a locked-rotor, how much current can it draw? 5-8 times the FLA ("Full-Load Amps," AKA: "FLA" or "The Nameplate Current")

33



34

What is the advantage of starting a motor in Wye verses Delta configuration? Wye LINE Current is 1/3 of Delta Current